

## Experiment # 1

Date(s):

### Verification of Kirchhoff's Laws

#### Aim:

To verify Kirchhoff's Voltage Law (KVL) and Kirchhoff's Current Law (KCL) for the given electrical network by making the circuit on a breadboard and using simulation.


#### Apparatus Required(software):

LTspice software

#### Apparatus Required(hardware):

Sl. No.	Components Name	Range	Quantity
1	Resistor	5.6 k $\Omega$ , 1 k $\Omega$ , 3.3 k $\Omega$	Each 1 No.
2	Voltmeter	0-30 V (DC)	3 Nos.
3	Ammeter	0-25mA (DC)	3 Nos.
4	RPS	0-32 V (DC)	2 Nos.
5	Connecting Wires	-	Few
6	Bread Board	-	1 No.

#### Circuit Diagram:

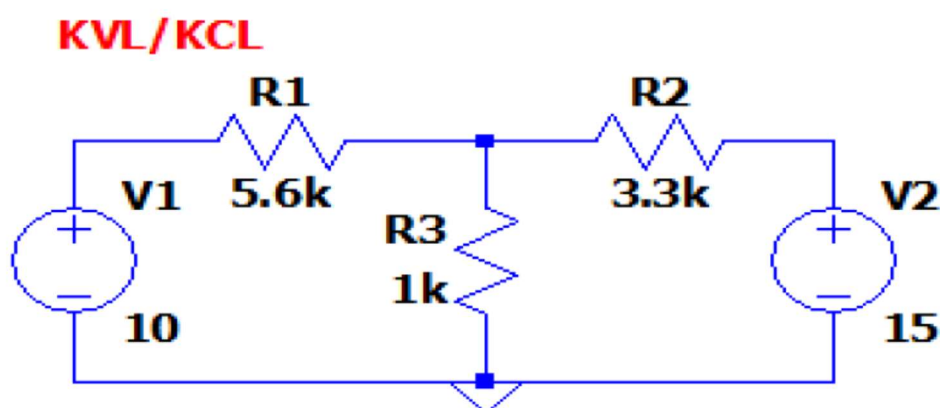

#### Theoretical Calculations:

By KCL, for 'N' currents meeting at a node

$$\sum_{n=1}^N i_n = 0$$

Let  $I_1$  = current through  $R_1$ ,

$I_2$  = current through  $R_2$ ,

$I_3$  = current through  $R_3$

Assuming  $I_1$  and  $I_2$  flow from  $V_1$  and  $V_2$  respectively, towards the node 'a' while  $I_3$  flows from the node 'a' to the ground, by KCL

$$I_1 + I_2 - I_3 = 0 \quad (1)$$

If  $V_{R1}$  = voltage across  $R_1$ ,

$V_{R2}$  = voltage across  $R_2$ ,


$V_{R3}$  = voltage across  $R_3$

Then by Ohm's law,

$$V_{R1} = I_1 * R_1 ;$$

$$V_{R2} = I_2 * R_2 ;$$

$$V_{R3} = I_3 * R_3$$

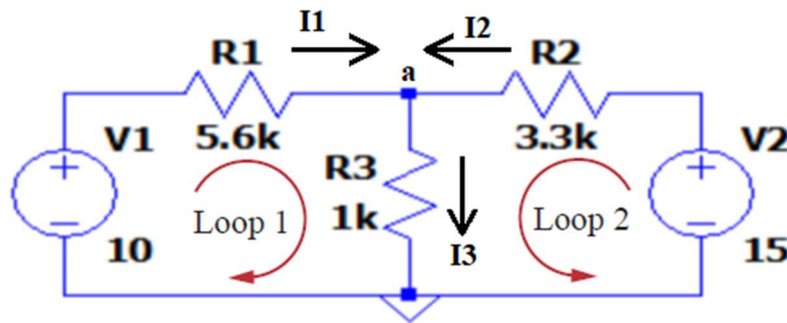

By KVL, for 'M' voltages in a closed loop

$$\sum_{m=1}^M v_m = 0$$

Applying KVL to loop 1,

$$-V_1 + V_{R1} + V_{R3} = 0$$

In terms of currents,

$$-V_1 + I_1 * R_1 + I_3 * R_3 = 0 \quad (2)$$

Applying KVL to loop 2,

$$-V_2 + V_{R2} + V_{R3} = 0$$

In terms of currents,

$$-V_2 + I_2 * R_2 + I_3 * R_3 = 0 \quad (3)$$

For  $R_1 = 5.6 \text{ k}\Omega$ ,  $R_2 = 3.3 \text{ k}\Omega$ ,  $R_3 = 1 \text{ k}\Omega$ , and  $V_1 = 10 \text{ V}$ ,  $V_2 = 15 \text{ V}$ , we have

$$I_1 + I_2 = I_3 \quad (4)$$

$$-10 + I_1 * 5600 + I_3 * 1000 = 0 \quad (5)$$

$$-15 + I_2 * 3300 + I_3 * 1000 = 0 \quad (6)$$

Substituting eq.(4) in eq.s (5) and (6), we get

$$I_1 * 5600 + (I_1 + I_2) * 1000 = 10 \rightarrow I_1 * 6600 + I_2 * 1000 = 10 \quad (7)$$

$$I_2 * 3300 + (I_1 + I_2) * 1000 = 15 \rightarrow I_1 * 1000 + I_2 * 4300 = 15 \quad (8)$$

Solving eq.s (7) and (8), we get


Branch currents,  $I_1 = 1.022 \text{ mA}$ ,  $I_2 = 3.25 \text{ mA}$ ,  $I_3 = I_1 + I_2 = 4.27 \text{ mA}$

Nodal voltages  $V_{R1} = I_1 * R_1 = 5.72 \text{ V}$ ,  $V_{R2} = I_2 * R_2 = 10.73 \text{ V}$ ,  $V_{R3} = I_3 * R_3 = 4.27 \text{ V}$ .

## **A. Software Experiment**
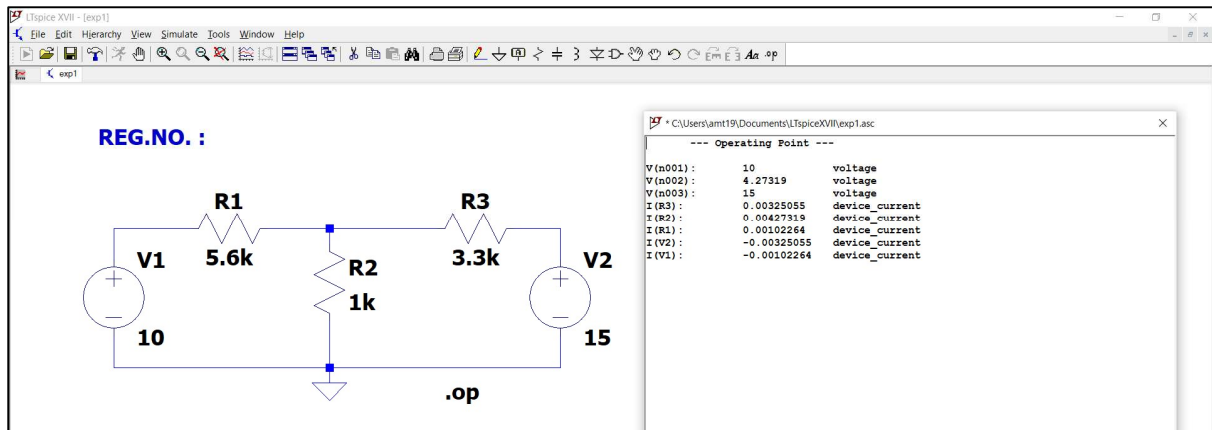
### **Procedure:**


- Open a new file.
- Select dc voltage source from components list. Track and paste it. Right click to feed voltage value.
- Take resistor from the components list. Right click to feed resistor value and rename the components as per the components name in circuit diagram.
- Connect the components using connector.
- Save the file.
- Edit simulate cmd. Choose dc op ppt.
- Run the file
- Results will be displayed. Verify it with theoretical value




## B. Hardware Experiment

### Connection Diagram:

#### 1) KCL

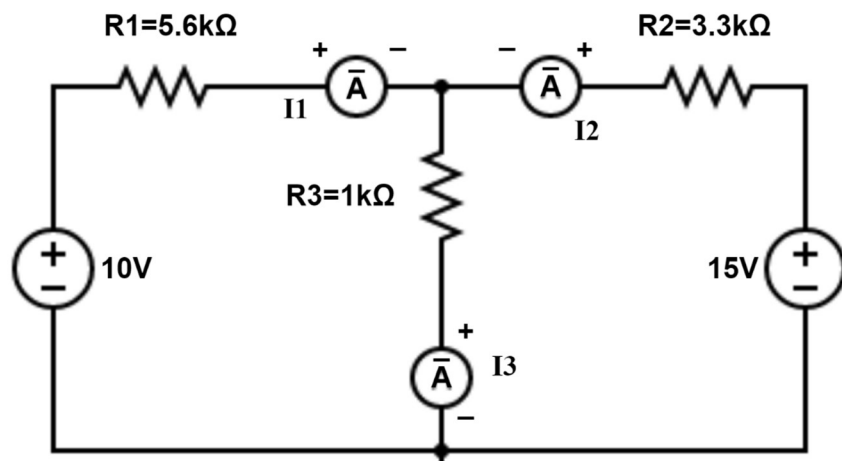

#### 2) KVL

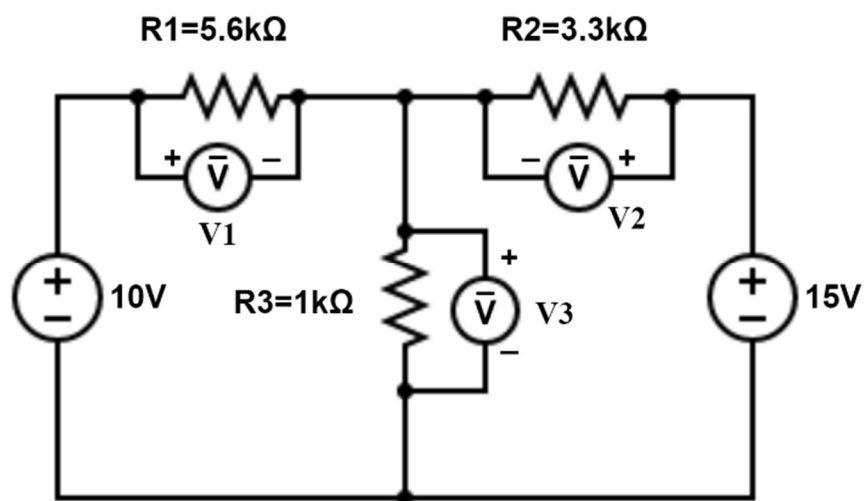

### Procedure:

#### KCL

- Connections are given as per circuit diagram.

- Supply voltage is given using regulated power supply.
- The ammeter readings are noted and tabulated.

#### KVL

- Connections are given as per circuit diagram.
- Supply voltage is given using regulated power supply.
- The voltmeter readings are noted and tabulated.

#### **Observations:**

S. No	Parameter to be measured	Value Measured with Units (Theoretical)	Value Measured with Units (Simulation)	Value Measured with Units (Practical)
1	Branch Current through 5.6 k $\Omega$			
2	Branch Current through 1 k $\Omega$			
3	Branch Current through 3.3 k $\Omega$			
4	Summation of currents at the junction of R1, R2 and R3			
5	Voltage across 5.6 k $\Omega$			
6	Voltage across 1 k $\Omega$			
7	Voltage across 3.3 k $\Omega$			
8	Algebraic sum of voltages in Mesh 1			
9	Algebraic sum of voltages in Mesh 2			

#### **Result:**

Thus, Kirchhoff's Laws were verified for the given electrical network using hardware and software setup.